

13.28 In addition, if the saturation resistance of the discharge BJT is $r_{\text{sat}}=20\Omega$, and $V_{\text{CE(on)}}=0.2\text{V}$, find the amount of time that it takes for the capacitor to discharge to 0.3V .

13.29

13.33

13.34

13.37

13.39